
 


Specification:

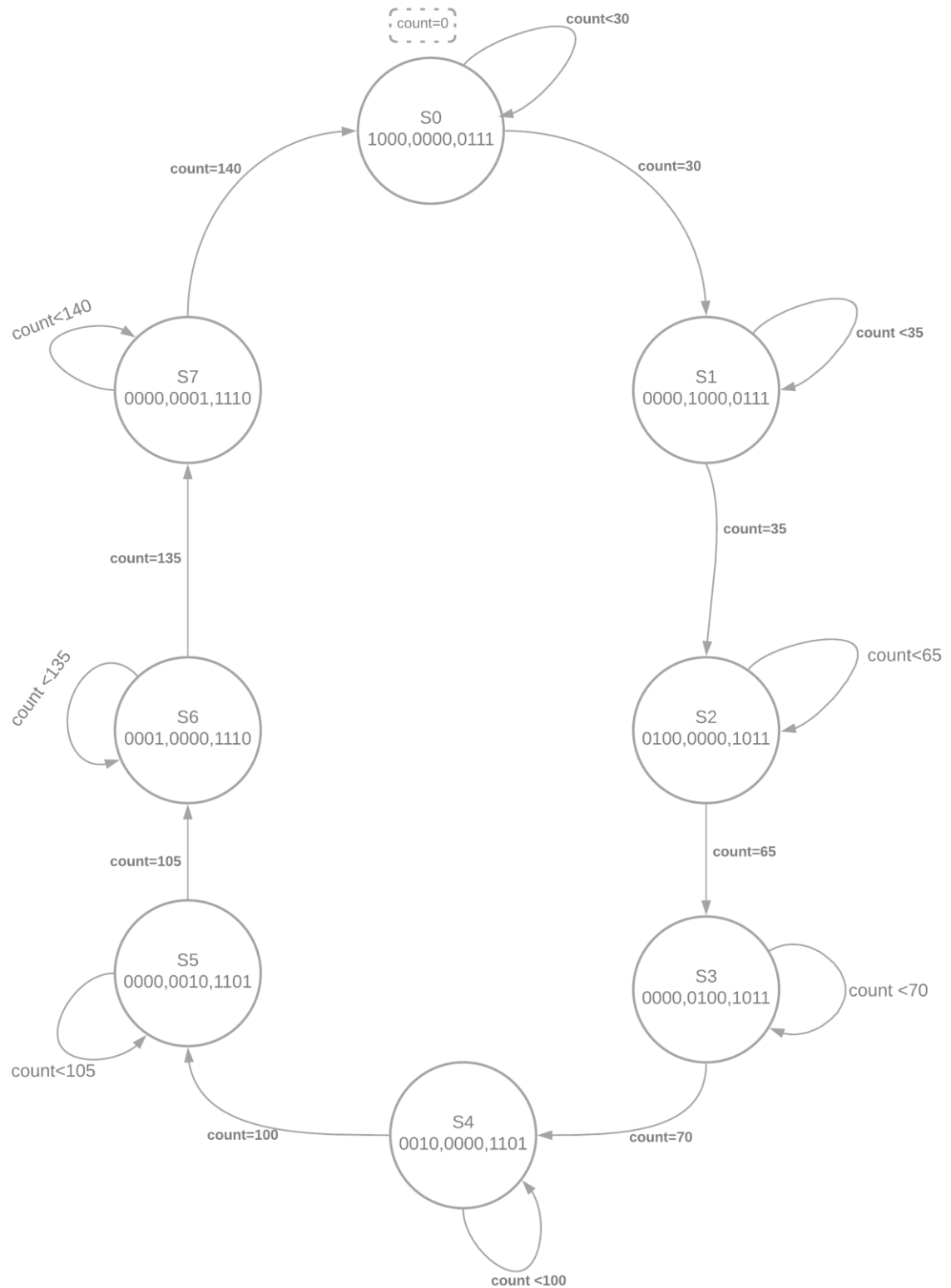

Our design is for a 4-way road. Each Direction (North , South ,east and west) got a traffic 3 colours each, Green ,yellow and red. No traffic for pedestrians implemented.

4-Way Traffic Light Controller State Diagram:



VHDL CODE:

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity traffic_light is
```

```
port ( clk : in std_logic;
```

```
      rst : in std_logic;
```

```
      green : out std_logic_vector(3 downto 0); --NESW
```

```
      red : out std_logic_vector(3 downto 0);-- NESW
```

```
      yellow: out std_logic_vector(3 downto 0)); --NESW
```

```
end traffic_light;
```

```
architecture Behavioral of traffic_light is
```

```
type state is (S0,S1,S2,S3,S4,S5,S6,S7);
```

```
signal currentstate: state := S0;
```

```
begin
```

```
counting: Process ( clk,rst)
```

variable count: integer := 0; -- Intialize count by 0

begin

if rst = '1' then

currentstate <= S0; -- remain at S0

count := 0;

else

if clk'event AND clk = '1' then

count := count +1;

if count<30 then -- from 0 to 30 seconds green light for North

currentstate <= S0;

elsif count>=30 AND count <35 then -- from 30s to 35s yellow light for North

currentstate <= S1;

elsif count >=35 AND count <65 then -- from 35s to 65s green light for East

currentstate <= S2;

elsif count >= 65 AND count <70 then -- from 65s to 70s yellow light for East

currentstate <= S3;

elsif count >=70 AND count <100 then -- from 70s to 100 green light for South

currentstate <= S4;

elsif count >= 100 AND count <105 then --from 100s to 105s yellow light for South

currentstate <= S5;

elsif count >= 105 AND count <135 then --from 105s to 135s green light for West

currentstate <= S6;

elsif count >= 135 AND count <140 then --from 135s to 140s yellow light for West

currentstate <= S7;

elsif count >= 140 then -- start again from state S0

count := 0;

END IF;

END IF;

END IF;

```
END PROCESS;
```

```
st : Process (currentstate)
```

```
begin
```

```
case currentstate is
```

```
when S0 => green <= "1000" ; yellow <= "0000" ; red <= "0111";
```

```
when S1 => green <= "0000" ; yellow <= "0100" ; red <= "0111";
```

```
when S2 => green <= "0100" ; yellow <= "0000" ; red <= "1011";
```

```
when S3 => green <= "0000" ; yellow <= "0100" ; red <= "1011";
```

```
when S4 => green <= "0010" ; yellow <= "0000" ; red <= "1101";
```

```
when S5 => green <= "0000" ; yellow <= "0010" ; red <= "1101";
```

```
when S6 => green <= "0001" ; yellow <= "0000" ; red <= "1110";
```

```
when S7 => green <= "0000" ; yellow <= "0001" ; red <= "1110";
```

```
when others => green <= "1000" ; yellow <= "0000" ; red <= "0111";
```

```
end case;
```

```
end process;
```

```
end Behavioral;
```

CODE EXPLANATION:

A 4 way traffic light is controlled by 5 signals clk,rst,green,yellow and red. Each direction North,East,South and West Traffic lights is controlled by 1 bit from the bit vector of green ,yellow and red signal.

Count is incremented whenever there's a clock. Counts keep on incrementing and its values is checked in the if conditions to Change from one state to another.

S0 = green light for North direction and red for others

S1= yellow light for North direction and red for others

S2= green light for East direction and red for others

S3= yellow light for East direction and red for others

S4= green light for South direction and red for others

S5= yellow light for South direction and red for others

S6= green light for West direction and red for others

S7= yellow light for West direction and red for others

In the second process

We take the current state as the sensitivity list and whenever the current state gets changed the current state signal triggers the green,yellow and red signals to change values. If state is anything else than the stated states (rst=1) then it stays at the first state which green light for north and red for others as S0

State Table:

Current State	Next State	Green	Yellow	Red
S0	S2	1000	0000	0111
S1	S3	0000	1000	0111
S2	S4	0100	0000	1011
S3	S5	0000	0100	1011
S4	S6	0010	0000	1101
S5	S6	0000	0010	1101
S6	S7	0001	0000	1110
S7	S0	0000	0001	1110

Test Bench:

```
LIBRARY IEEE;
USE IEEE.STD_LOGIC_1164.ALL;

entity Testbench is
end entity;

architecture tb of Testbench is

    signal green: std_logic_vector (3 downto 0);
    signal yellow : std_logic_vector (3 downto 0);
    signal red : std_logic_vector (3 downto 0);
    signal clk,rst: std_logic;

    begin

        DUT : ENTITY work.traffic_light

        PORT MAP(
            green => green,
            yellow => yellow,
            red => red,
            clk => clk,
            rst => rst );

        Clock : process
        begin
            clk <= '0';
            wait for 1 ns;
            clk <= '1';
            wait for 1 ns;
        end process;
```


```
stimulis : process  
begin  
report("Starting simulation");  
rst <= '1'; wait for 20 ns;  
rst <= '0'; wait for 200000 ns;  
report("End simulation");  
end process;  
end architecture;
```

Test Bench Explanation:

Clk is every 1 nanosecond and therefore count is incremented every 1 nanosecond

Also, the first 20 ns the rst signal is 1 and so we could see the output is S0 according to the code

Output Waveform:

 

The first 20ns `rst=1` and so `state=S0`

Then `rst= 0` and states start changing

